


## CME1214 Logic Design Homework 2

## **Experiment 1**

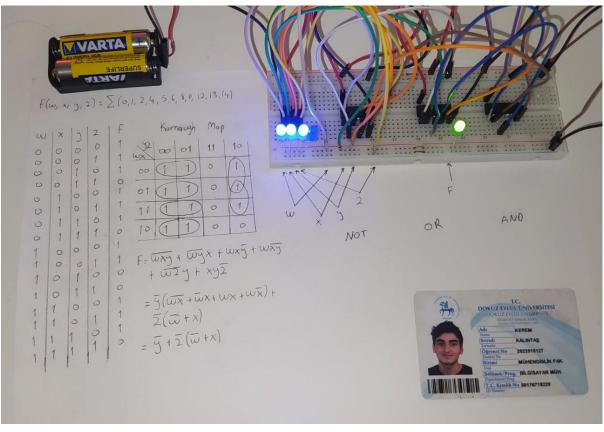

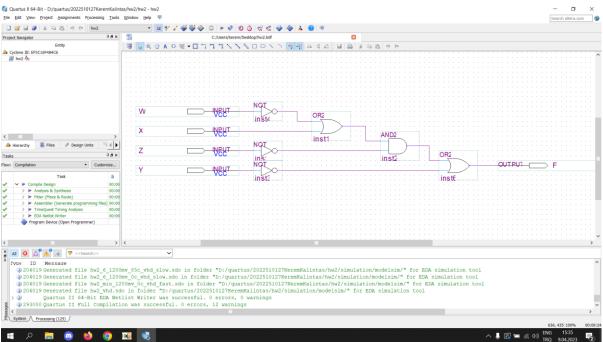

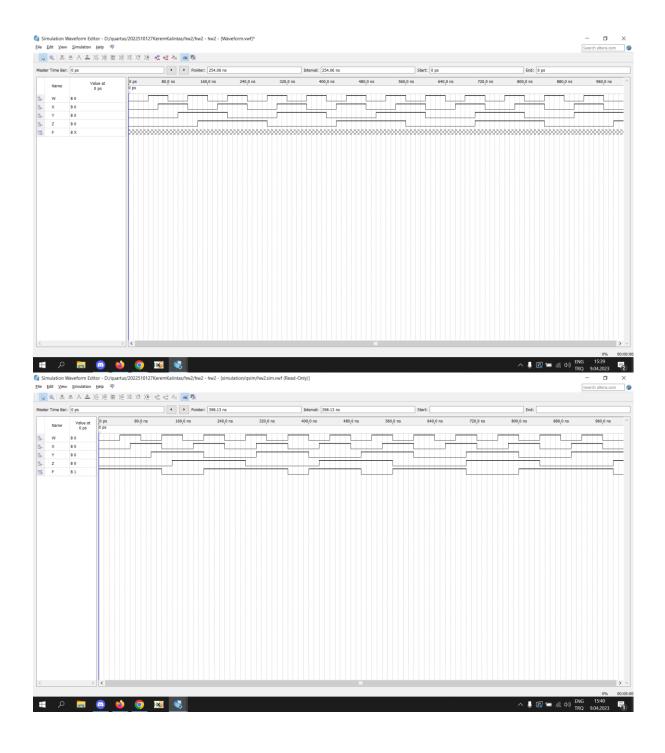

## **Experiment 2**

