



## CME1214 Logic Design Homework 4

Divide-by-2 using a D Flip Flop

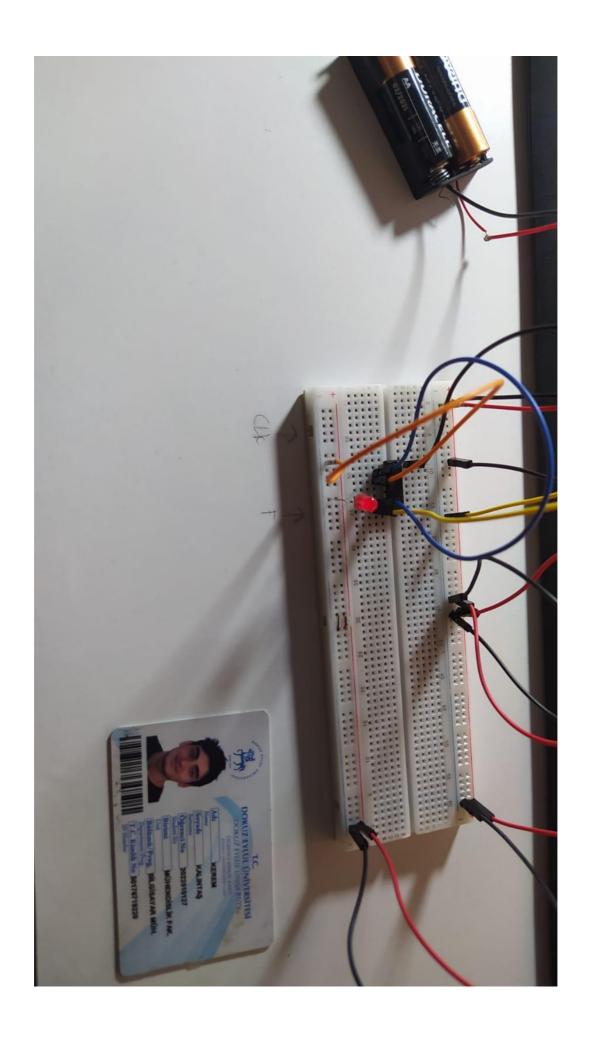


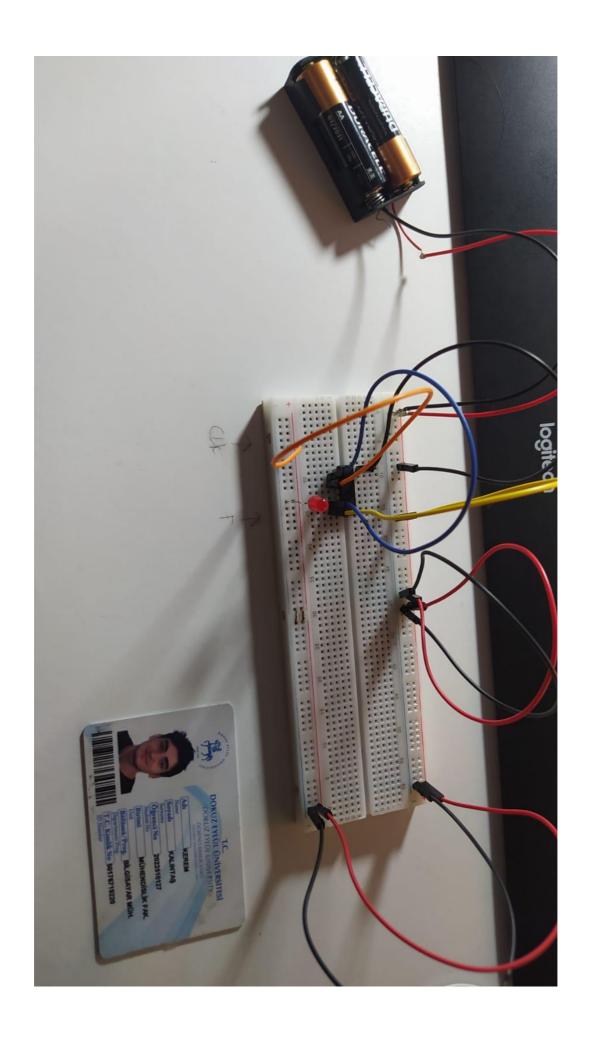


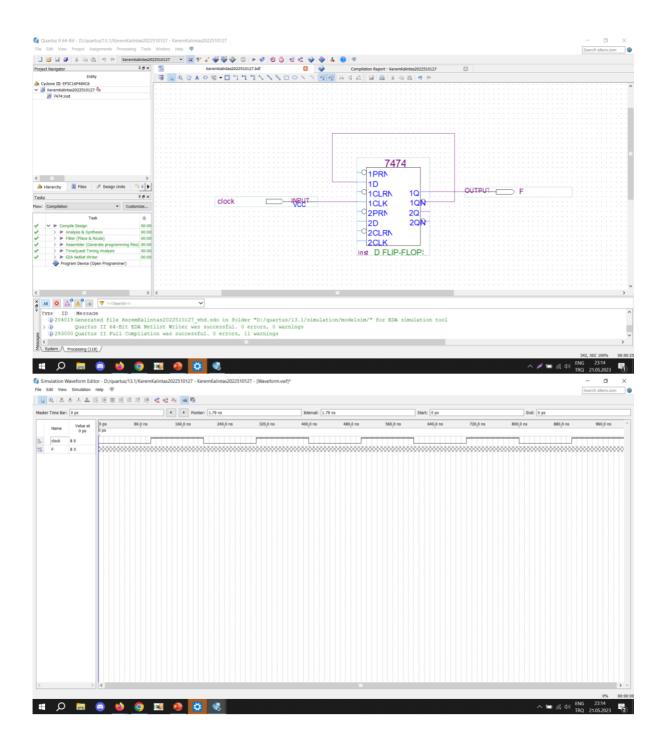


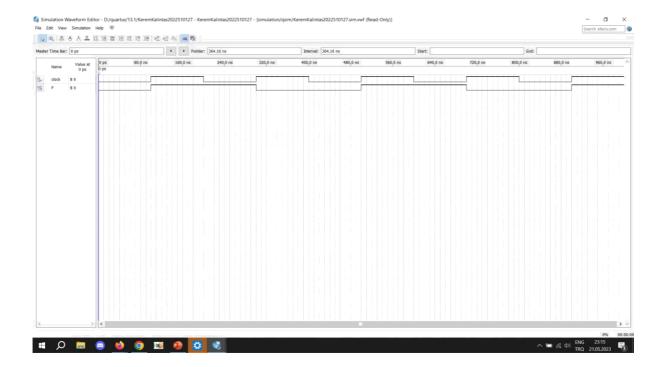


## Divide-by-4 using D flip flops

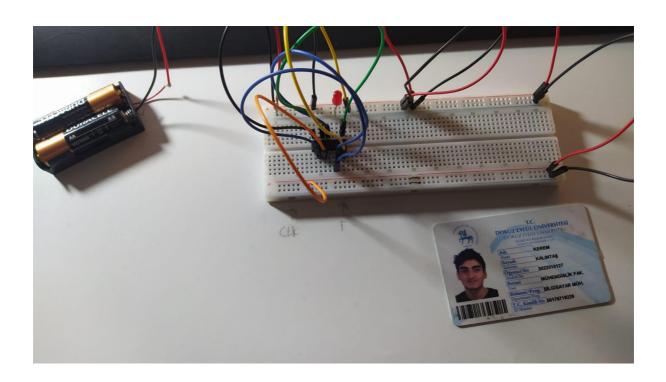


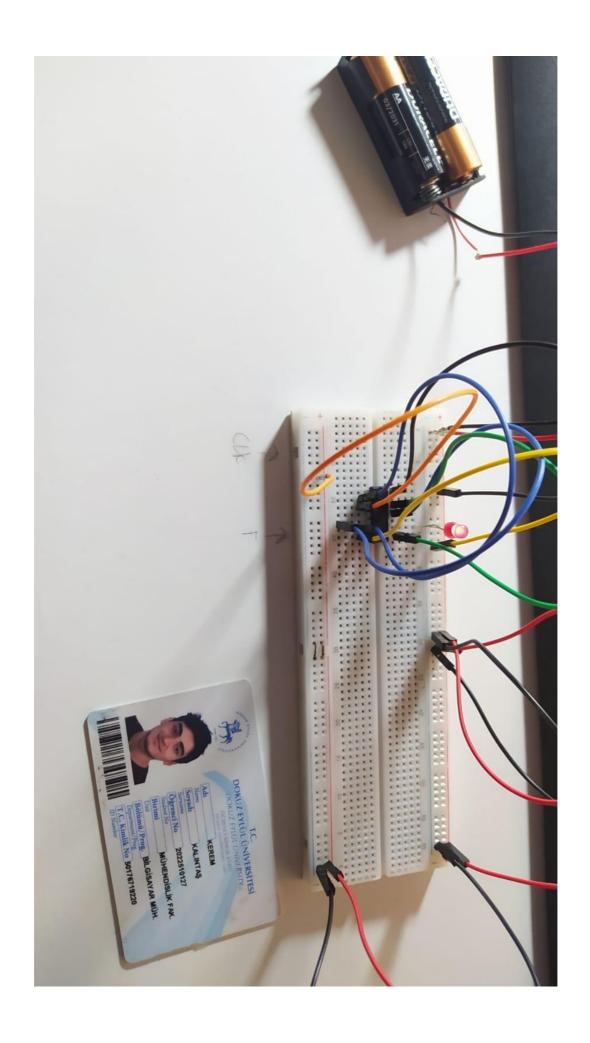


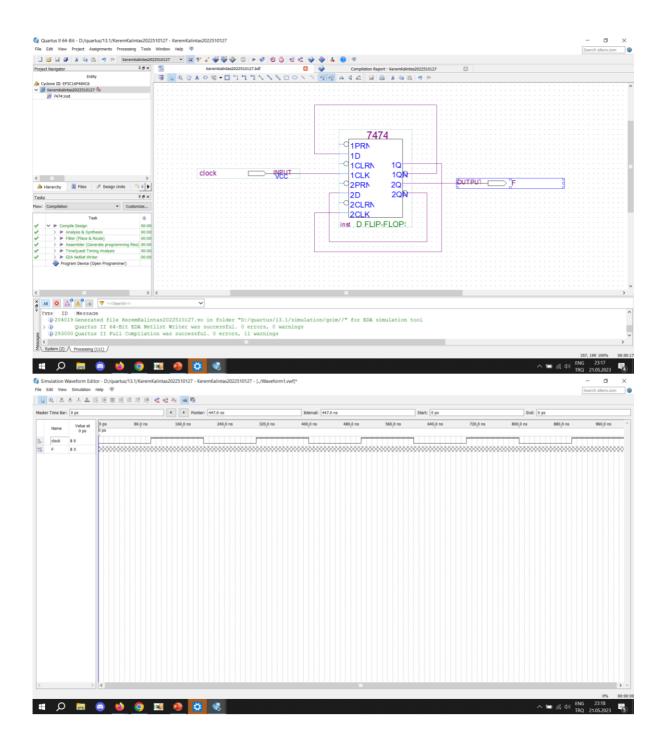


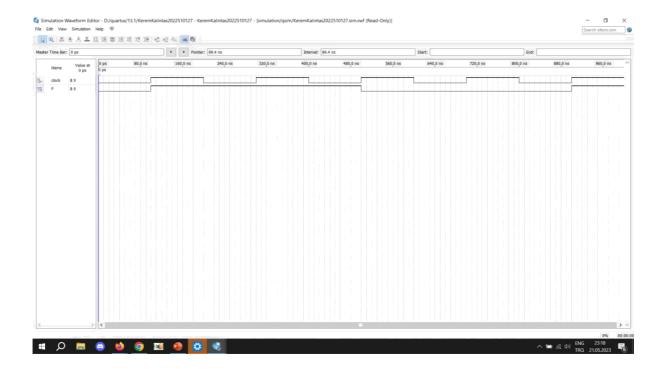


## Divide-by-2 using a JK Flip Flop

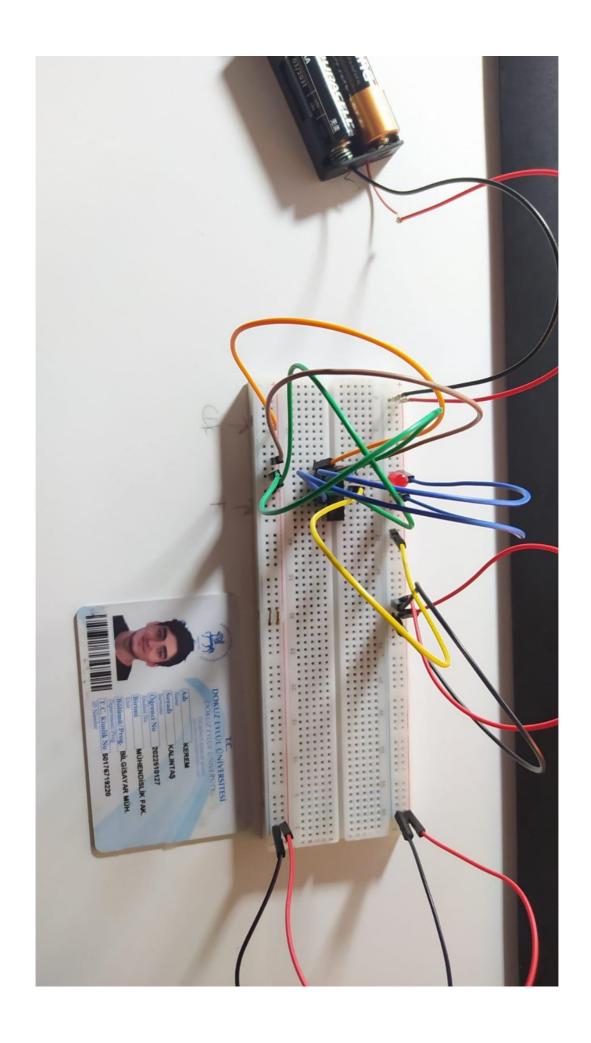

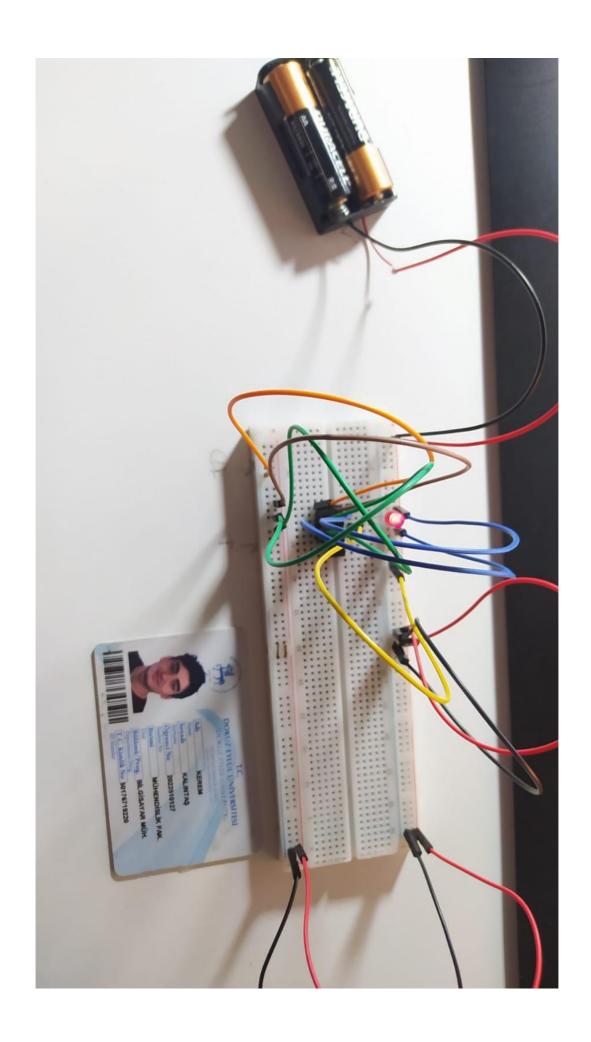

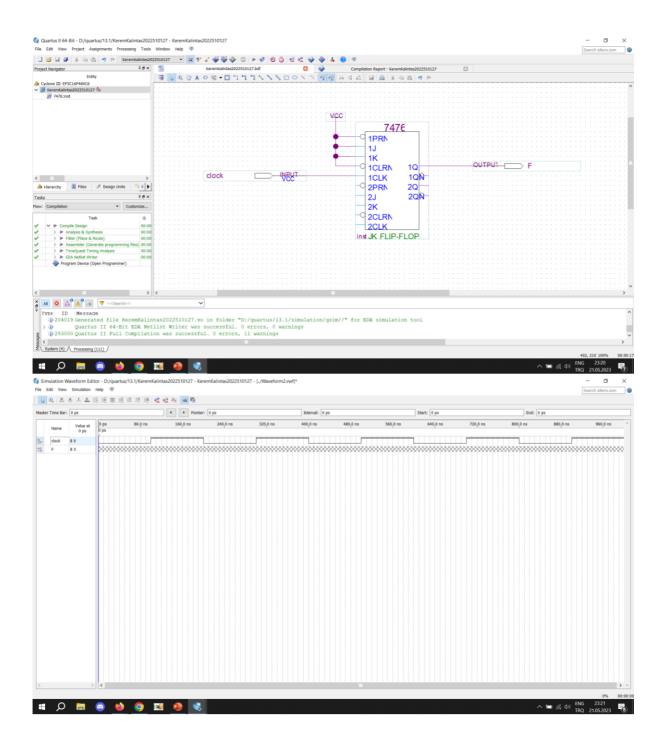

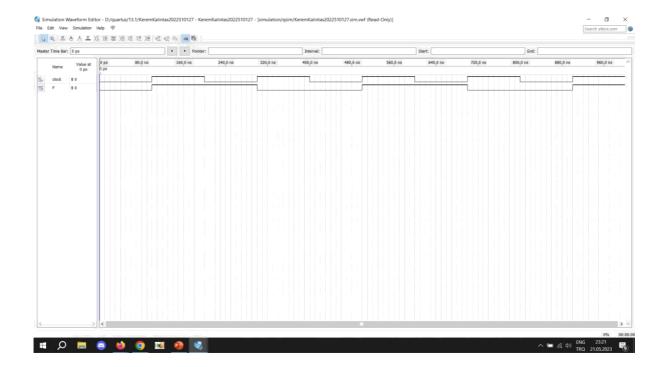

## Divide-by-4 using JK Flip Flops

