

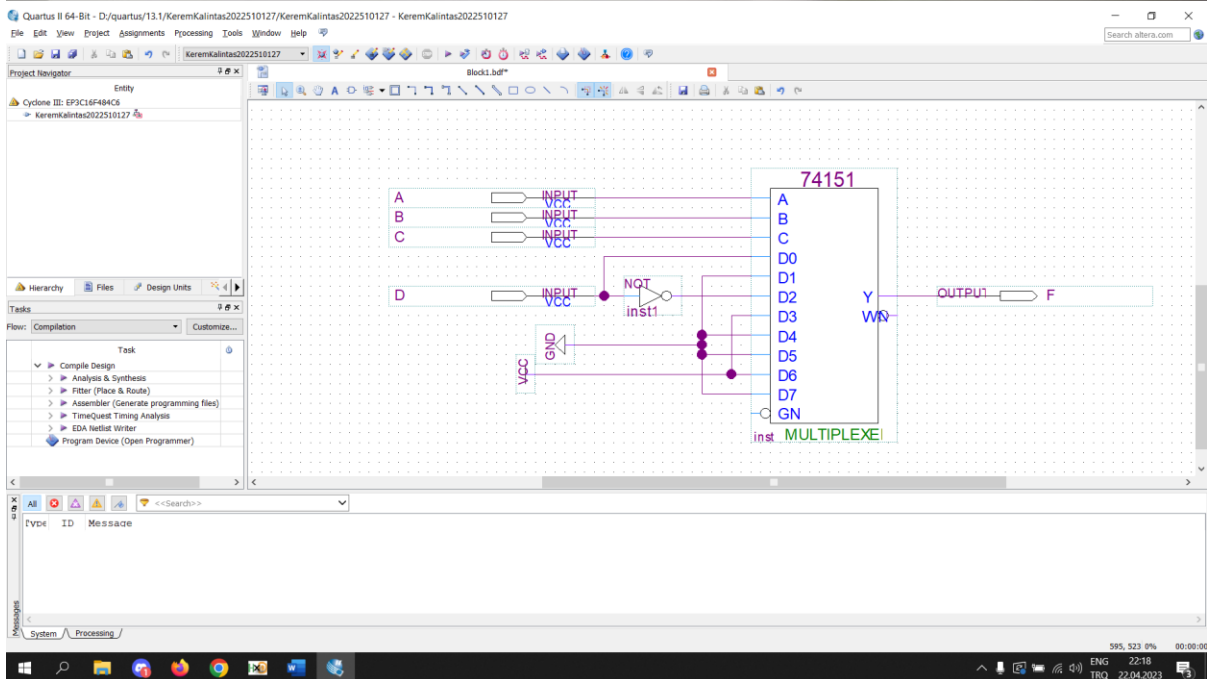
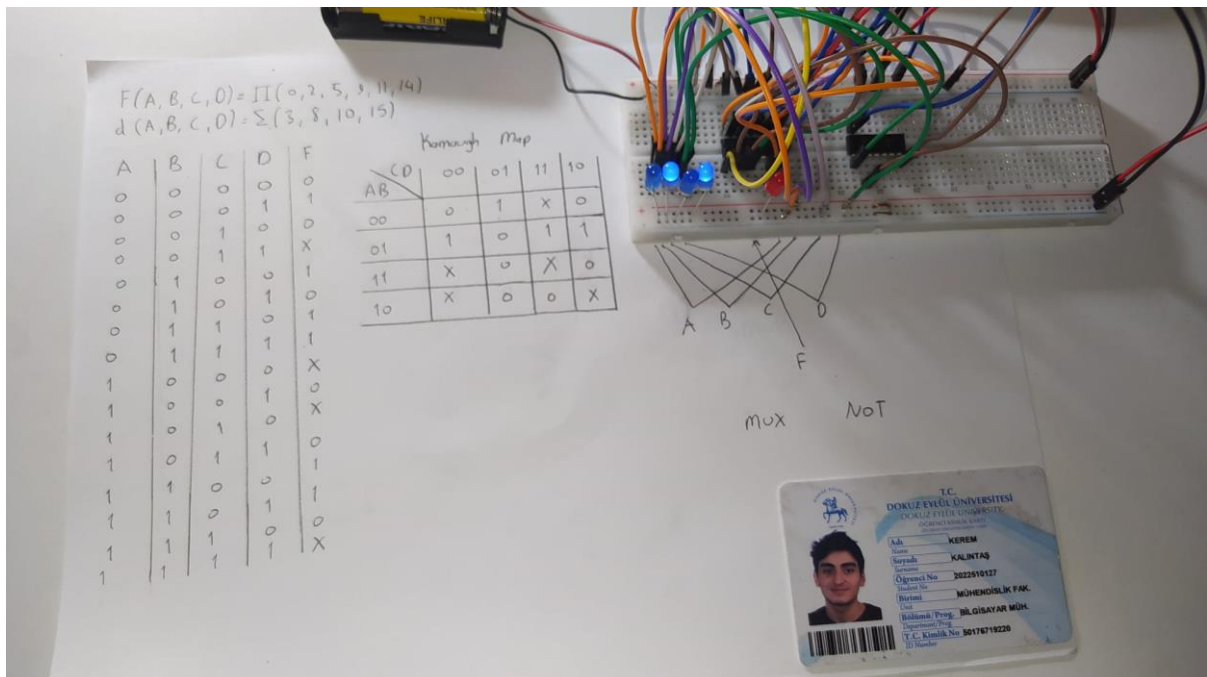




CME1214 Logic Design Homework 3


Experiment 1

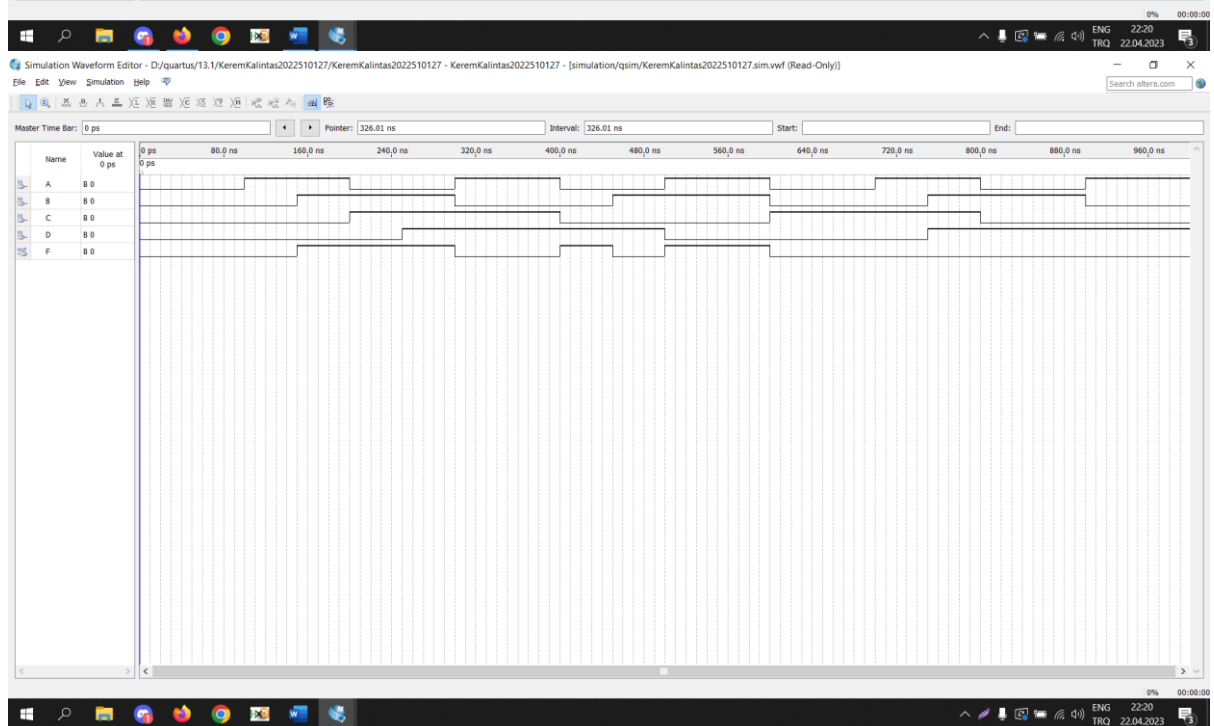

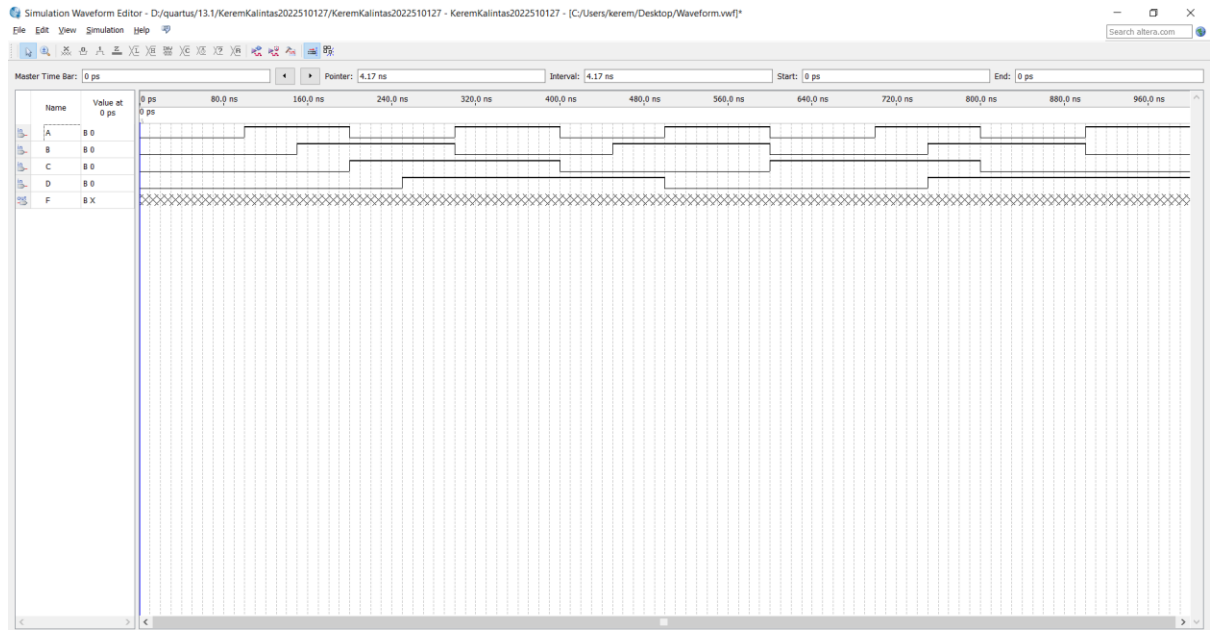

Experiment 2

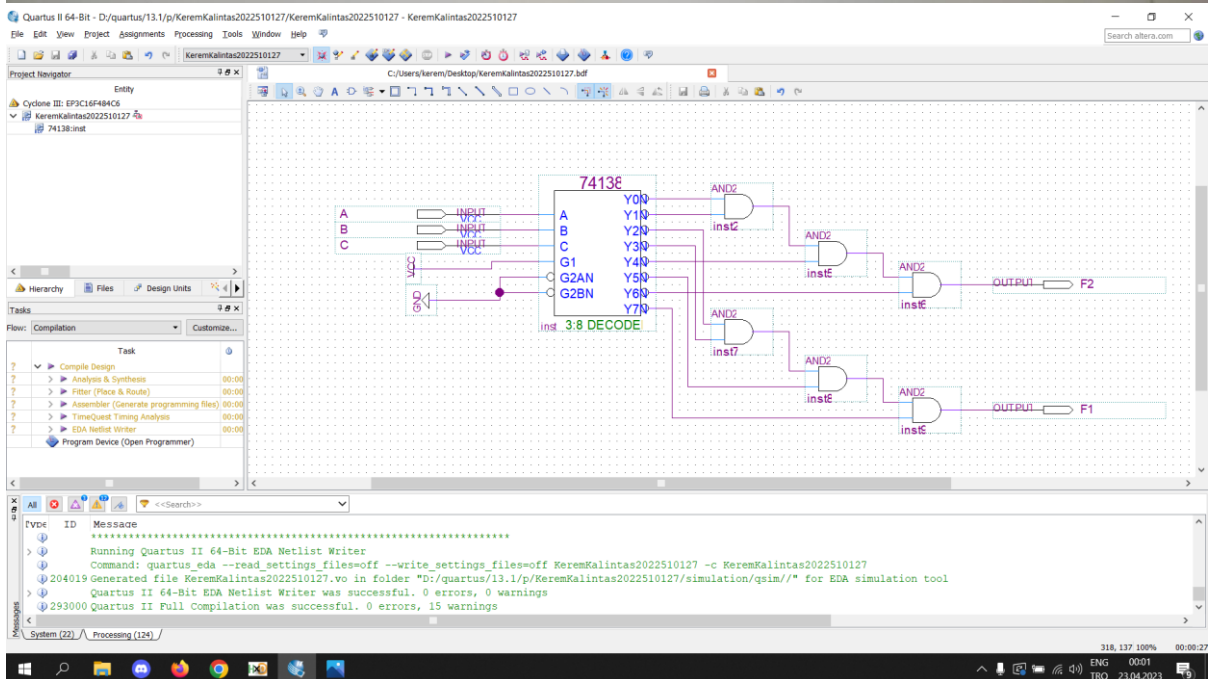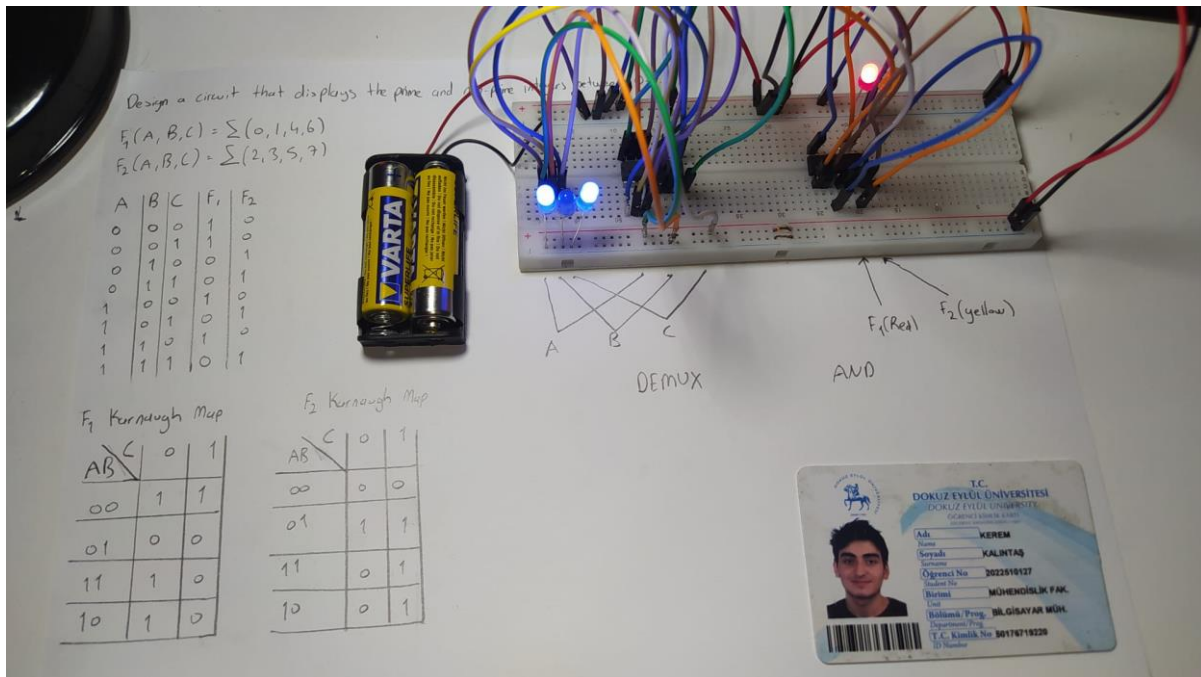

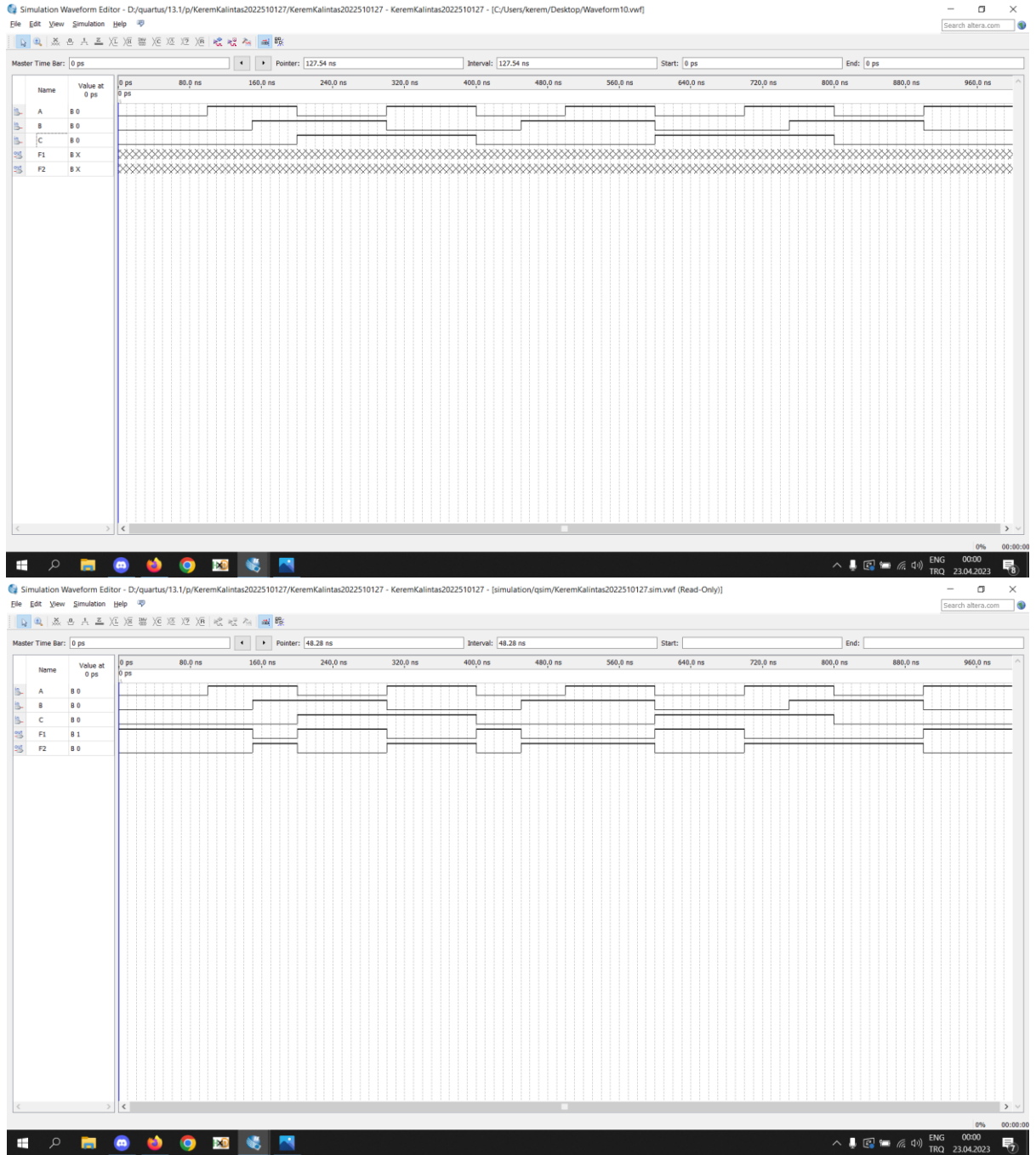

Kerem Kalintas 2022510127